


Classical Control Systems

Homework 01

Do the following problems and show all your work for full credit. Note: not all problems will be graded, however, you must complete all problems to get full credit.

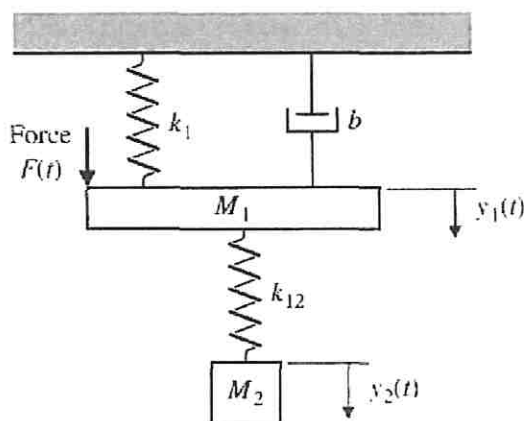Problem 1

Find the equations of motion (differential equations) that describes the behavior of the following mechanical system:





y
 (t) positive direction chosen same as direction of applied force.

* start by assuming that $y_2(t) > y_1(t)$ and positive displacement direction is down (see arrow above).

* Because $y_2(t) > y_1(t)$, spring k_{12} is in tension!

* Now we draw FBD:

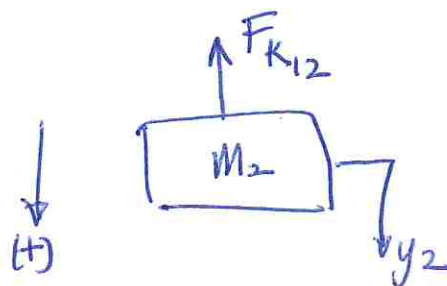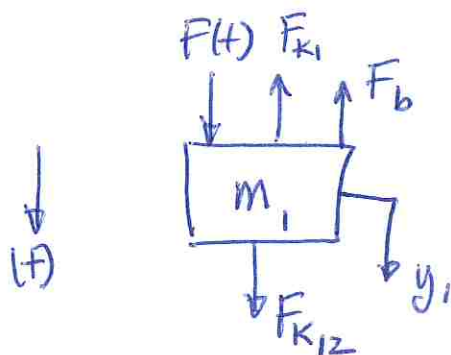

Note: gravity force is left out because it does not affect dynamics!

* Now we sum forces and apply Newton's 2nd law: (2)

for mass m_1 :

$$\sum F = m_1 \ddot{y}_1(t)$$

$$\Rightarrow F(t) - F_{K_1} - F_b + F_{K_{12}} = m_1 \ddot{y}_1(t)$$

sub in the forces for springs and damper:

$$F(t) - K_1 y_1(t) - b \dot{y}_1(t) + K_{12} (y_2(t) - y_1(t)) = m_1 \ddot{y}_1(t)$$

rearrange into standard O.D.E form:

$$m_1 \ddot{y}_1(t) + b \dot{y}_1(t) + (K_1 + K_{12}) y_1(t) - K_{12} y_2(t) = F(t)$$

for mass m_2 :

$$\sum F = m_2 \ddot{y}_2(t)$$

$$\Rightarrow -F_{K_{12}} = m_2 \ddot{y}_2(t)$$

$$-K_{12} (y_2(t) - y_1(t)) = m_2 \ddot{y}_2(t)$$



rearrange:

$$m_2 \ddot{y}_2(t) + K_{12} y_2(t) - K_{12} y_1(t) = 0$$

Both of these equations describe the dynamics of the two-mass system,

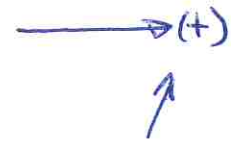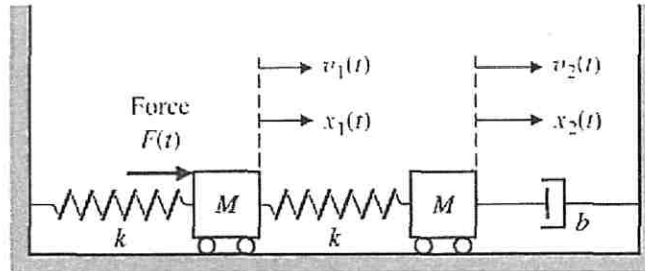Problem 2

Find the equations of motion (differential equations) that describes the behavior of the following mechanical system (note, both masses are the same):





choose positive direction so it is consistent w/ applied force.

* Start by assuming that $x_2(t) > x_1(t)$ and the positive direction is to the right.

* Because $x_2(t) > x_1(t)$, middle spring is in tension!

* Now we draw FBD:

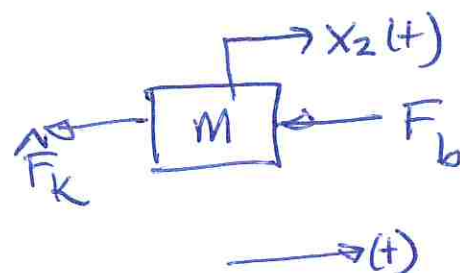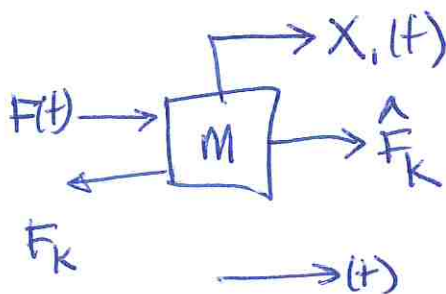

* Now apply Newton's 2nd Law and sum forces:

For the left mass:

$$\sum F = m \ddot{x}_1(t)$$

$$\Rightarrow F(t) - F_K + \hat{F}_K = m \ddot{x}_1(t)$$

(4)

sub in for the forces:

$$F(t) - Kx_1(t) + K(x_2(t) - x_1(t)) = m\ddot{x}_1(t)$$

rearrange:

$$m\ddot{x}_1(t) + 2Kx_1(t) - Kx_2(t) = F(t)$$

For the right mass:

$$\sum F = m\ddot{x}_2(t)$$

$$-\hat{F}_K - F_b = m\ddot{x}_2(t)$$

$$-K(x_2(t) - x_1(t)) - b\dot{x}_2(t) = m\ddot{x}_2(t)$$


rearrange:

$$m\ddot{x}_2(t) + b\dot{x}_2(t) + Kx_2(t) - Kx_1(t) = 0$$

Both of the above equations describe the dynamics of the system.

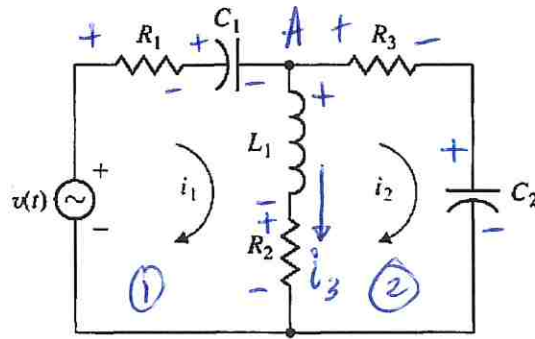Problem 3

Find the integral-differential (integro-differential) equations that governs the behavior of the following circuit. Note that the input is the voltage $v(t)$ and the output variables are the currents i_1 and i_2 . Your result should be differential equation(a), time-domain equations, that include these variables.



* Assume that i_1 flows through $R_1 + C_1$ and i_2 flows through R_3 and C_2 , so at node A, we have the following KCL:

$$\dot{i}_1 = \dot{i}_3 + \dot{i}_2$$

* Next, we add "+" and "-" signs associated with current flow through each element.

* Now, we apply the voltage loop equation (KVL):

Loop ①: $\sum V_i = 0$

$$\Rightarrow -v(t) + R_1 \dot{i}_1 + \frac{1}{C_1} \int \dot{i}_1 dt + L_1 \frac{d\dot{i}_3}{dt} + R_2 \dot{i}_3 = 0$$

we can sub in for \dot{i}_3 using KCL above, so

$$\Rightarrow -v(t) + R_1 \dot{i}_1 + \frac{1}{C_1} \int \dot{i}_1 dt + L_1 \frac{d}{dt}(\dot{i}_1 - \dot{i}_2) + R_2(\dot{i}_1 - \dot{i}_2) = 0$$

rearrange to get:

(6)

$$R_1 \dot{i}_1 + \frac{1}{C_1} \int i_1 dt + L_1 \frac{d}{dt} (i_1 - i_2) + R_2 (i_1 - i_2) = V(t)$$

For loop (2):

$$\sum V_i = 0$$

$$\Rightarrow R_3 \dot{i}_2 + \frac{1}{C_2} \int i_2 dt - R_2 \dot{i}_3 - L_1 \frac{d}{dt} \dot{i}_3 = 0$$


sub in for $i_3 = i_1 - i_2$ from KCL:

$$\Rightarrow R_3 \dot{i}_2 + \frac{1}{C_2} \int i_2 dt - R_2 (\dot{i}_1 - \dot{i}_2) - L_1 \frac{d}{dt} (\dot{i}_1 - \dot{i}_2) = 0$$


Both of these equations describe the dynamics of the system. They are integro-diff. equations in terms of i_1 and i_2 with $V(t)$ as the input!

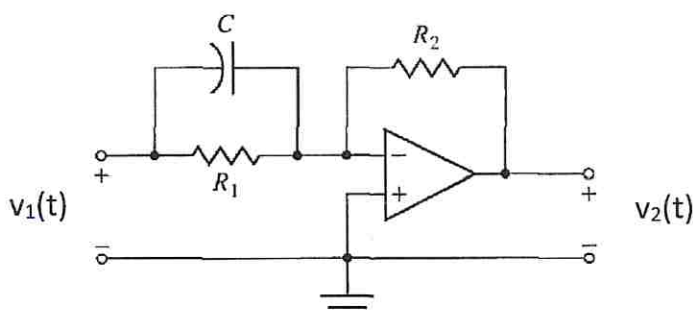Problem 4

For the following op-amp circuit, find the differential equation that relates the input $v_1(t)$ to the output voltage $v_2(t)$:



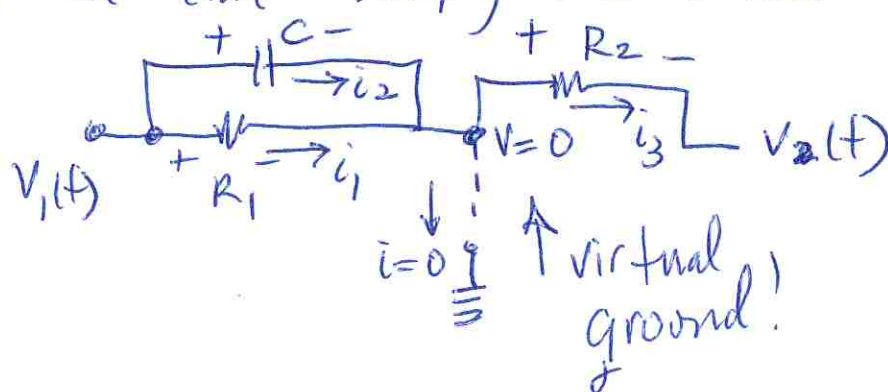* First, this op-amp circuit is in negative feedback, so we can simplify the circuit to:



Did this w/ the 2 rules for neg. FB op-amps!

* To find relationship between $v_1(t)$ and $v_2(t)$, we first notice that:

$$i_1 + i_2 = i_3 \quad (\text{KCL})$$

* Next, we can find each current w/ element equations:

$$v_1(t) - 0 = R_1 i_1 \Rightarrow \underline{\underline{i_1 = \frac{v_1(t)}{R_1}}}$$

(8)

$$V_1(t) - 0 = \frac{1}{C} \int i_2 dt$$

Take derivative of both sides to get

$$\dot{V}_1(t) = \frac{1}{C} i_2 \Rightarrow \underline{i_2 = C \dot{V}_1(t)}$$

Finally: $0 - V_2(t) = R_2 i_3 \Rightarrow \underline{i_3 = -\frac{V_2(t)}{R_2}}$

Now go back to KCL:

$$i_1 + i_2 = i_3$$

sub into this equation the currents:

$$\frac{V_1(t)}{R_1} + C \dot{V}_1(t) = -\frac{V_2(t)}{R_2}$$

rearrange into stand o.d.e form:

$$-\frac{1}{R_2} V_2(t) = C \dot{V}_1(t) + \frac{1}{R_1} V_1(t)$$

$$\Rightarrow \boxed{\frac{1}{R_2} V_2(t) = -C \dot{V}_1(t) - \frac{1}{R_1} V_1(t)}$$

Problem 5

Consider the following system where a human operator is part of the closed-loop control system. Sketch the block diagram of the valve control system and label the signals and blocks.

