


### 3. Pre-Lab Exercises

- In lecture, we showed how to derive the transfer function of an RC circuit using impedances. Use this method to derive equations (5) and (6).

Low Pass: 
$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j(\omega / \omega_c)} = \frac{1}{1 + j(f / f_c)} \quad (5)$$

High Pass: 
$$\frac{V_{out}}{V_{in}} = \frac{j(\omega / \omega_c)}{1 + j(\omega / \omega_c)} = \frac{j(f / f_c)}{1 + j(f / f_c)} \quad (6)$$

Low Pass:

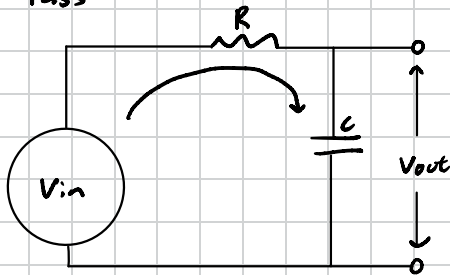


Total impedance:  $R + \frac{1}{j\omega C}$   
 $i = \frac{V_{in}}{Z} = \frac{V_{in}}{R + \frac{1}{j\omega C}}$

$$V_{out} = i Z_C = \frac{V_{in}}{R + \frac{1}{j\omega C}} \left( \frac{1}{j\omega C} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega R C}$$

$$\frac{1}{RC} = \omega_c \therefore \Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\left(\frac{\omega}{\omega_c}\right)} = \frac{1}{1 + j\left(\frac{f}{f_c}\right)}$$

High Pass

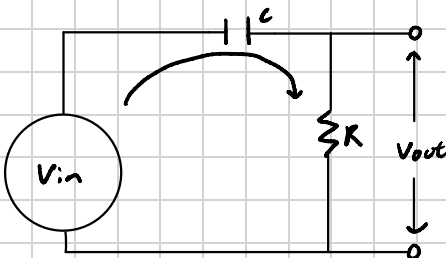

Total impedance:  $R + \frac{1}{j\omega C}$   
 $i = \frac{V_{in}}{Z} = \frac{V_{in}}{R + \frac{1}{j\omega C}}$

$$V_{out} = i R_C = \frac{V_{in}}{R + \frac{1}{j\omega C}} (R)$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{R j\omega C}{R j\omega C + 1}$$

$$\frac{1}{RC} = \omega_c \therefore \Rightarrow \frac{V_{out}}{V_{in}} = \frac{j\left(\frac{\omega}{\omega_c}\right)}{j\left(\frac{\omega}{\omega_c}\right) + 1} = \frac{j\left(\frac{f}{f_c}\right)}{1 + j\left(\frac{f}{f_c}\right)}$$

2. Show how equations (8) and (9) can be derived from equations (5) and (6). Hint: a complex number  $a + bj$  has magnitude  $\sqrt{a^2 + b^2}$  and phase angle of  $\tan^{-1}\left(\frac{b}{a}\right)$ .

Low Pass:  $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (f/f_c)^2}}, \quad \phi = -\tan^{-1}\left(\frac{f}{f_c}\right)$  (8)

High Pass:  $\left| \frac{V_{out}}{V_{in}} \right| = \frac{f/f_c}{\sqrt{1 + (f/f_c)^2}}, \quad \phi = \tan^{-1}\left(\frac{f_c}{f}\right)$  (9)

Low Pass:

(5)  $\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\left(\frac{f}{f_c}\right)}$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\sqrt{1^2}}{\sqrt{1^2 + \left(j\left(\frac{f}{f_c}\right)\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$\phi = \tan^{-1}\left(\frac{\text{imaginary}}{\text{real}}\right)_{\text{numerator}} - \tan^{-1}\left(\frac{\text{imaginary}}{\text{real}}\right)_{\text{denominator}}$

$\phi = \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left(\frac{\left(\frac{f}{f_c}\right)}{1}\right)$

$\phi = 0 - \tan^{-1}\left(\frac{f}{f_c}\right)$

$\phi = -\tan^{-1}\left(\frac{f}{f_c}\right)$

High Pass:

(6)  $\frac{V_{out}}{V_{in}} = \frac{j\left(\frac{f}{f_c}\right)}{1 + j\left(\frac{f}{f_c}\right)}$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\sqrt{\left(j\left(\frac{f}{f_c}\right)\right)^2}}{\sqrt{1^2 + \left(j\left(\frac{f}{f_c}\right)\right)^2}} = \frac{f/f_c}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$\frac{j\left(\frac{f}{f_c}\right)}{1 + j\left(\frac{f}{f_c}\right)} \left( \frac{1 - j\left(\frac{f}{f_c}\right)}{1 - j\left(\frac{f}{f_c}\right)} \right) = \frac{j\left(\frac{f}{f_c}\right) + \left(\frac{f}{f_c}\right)^2}{1 + \left(\frac{f}{f_c}\right)^2}$

$\phi = \tan^{-1}\left(\frac{\text{imaginary}}{\text{real}}\right)_{\text{numerator}} - \tan^{-1}\left(\frac{\text{imaginary}}{\text{real}}\right)_{\text{denominator}}$

$\phi = \tan^{-1}\left(\frac{f/f_c}{f^2/f_c^2}\right) - \tan^{-1}\left(\frac{0}{1}\right)$

$\phi = \tan^{-1}\left(\frac{\frac{f}{f_c}}{\frac{f^2}{f_c^2}}\right) = \tan^{-1}\left(\frac{f_c}{f}\right)$

$\phi = \tan^{-1}\left(\frac{f_c}{f}\right)$


3. Using equations (8), (9) and (10), plot the frequency response of a low and high pass filter using the parameters indicated below. Calculate the Magnitude (dB) and phase (deg) for a range of logarithmically-spaced frequencies spanning 2 orders of magnitude above and below cut-off frequency (hint: use *logspace* function in MATLAB). Be sure to plot the frequencies on a log scale (i.e. *semilogx* in MATLAB) and properly label your axes. Also label the cut-off frequency on your plot. Include screenshots of your code and plots in line with this question with your name indicated. Also submit your .m files to canvas.

a. Low-Pass filter with  $R = 4.7 \text{ k}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$



b. High-Pass filter with  $R = 4.7 \text{ k}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$



Frequency Response Plot of a Low-Pass Filter | Brandon Lim U1244501

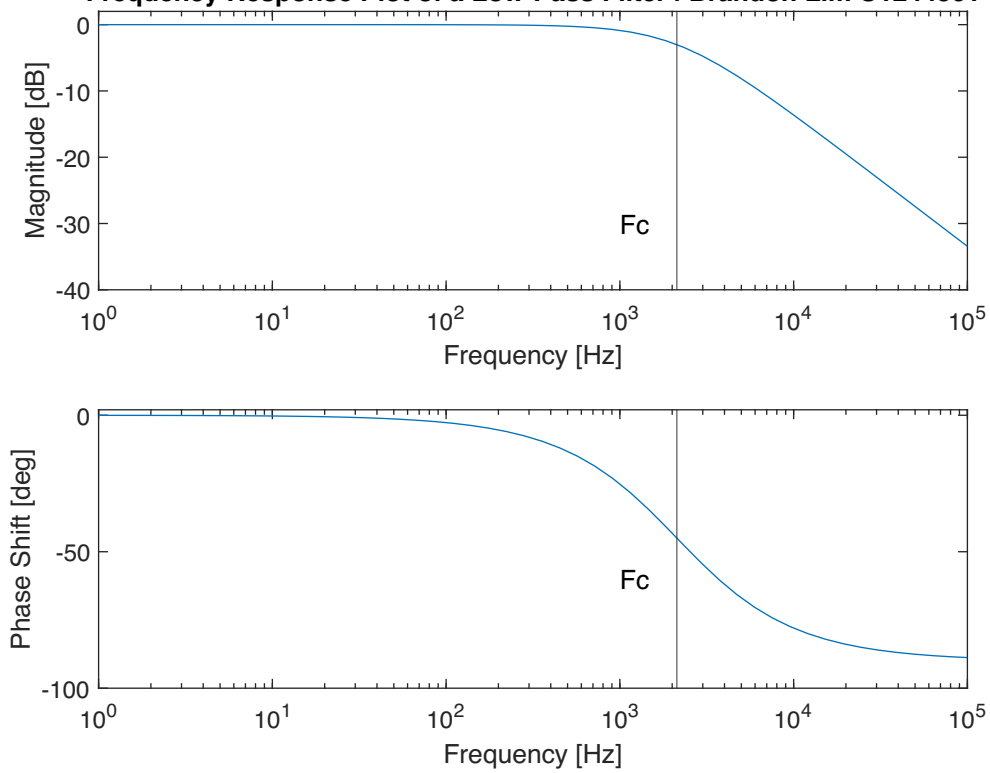

Frequency Response Plot of a High-Pass Filter | Brandon Lim U1244501

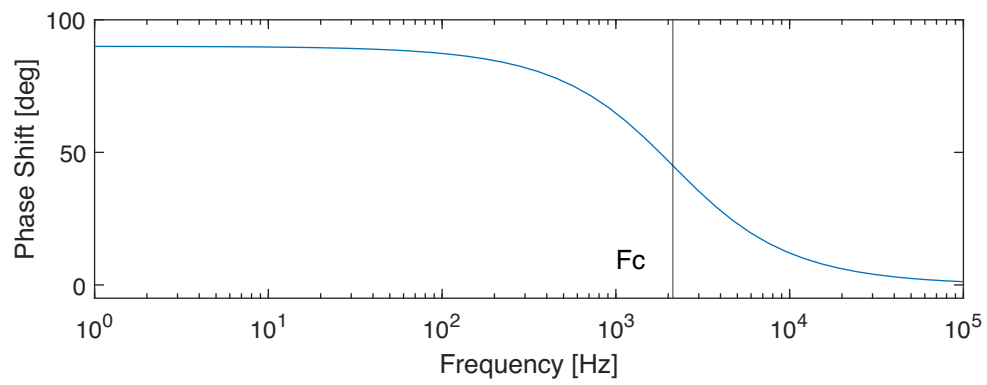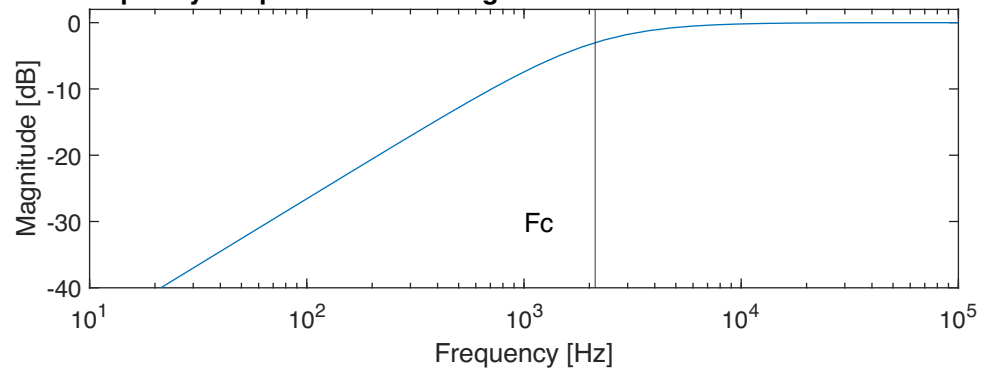

```
% Brandon Lim
clear, clc, close all
%Low Pass Filter
w = logspace(0,5);
R = 4.7*1000; %ohms
C = 0.1 * 10^-6; %farads

wc = 1/(R*C); %Cutoff Frequency
magnitudeNorm = 1./sqrt(1+((w.^2)/(wc.^2)));
magnitudeDB = 20*log10(magnitudeNorm);

phaseShift = -atan(w./wc) .* 180./pi;

figure
subplot(2,1,1)
semilogx(w,magnitudeDB)
ylim([-40,2])
title("Frequency Response Plot of a Low-Pass Filter | Brandon Lim U1244501")
xlabel("Frequency [Hz]")
ylabel("Magnitude [dB]")
hold on
subplot(2,1,1)
xline(wc)
text(10^3,-30,0,"Fc")

subplot(2,1,2)
semilogx(w,phaseShift)
ylim([-100,2])
xlabel("Frequency [Hz]")
ylabel("Phase Shift [deg]")
hold on
subplot(2,1,2)
xline(wc)
text(10^3,-60,0,"Fc")
%% High Pass
clear, clc, close all
w = logspace(0,5);
R = 4.7*1000; %ohms
C = 0.1 * 10^-6; %farads

wc = 1/(R*C); %Cutoff Frequency
magnitudeNorm = (w./wc)./(sqrt(1+((w.^2)/(wc.^2))));
magnitudeDB = 20*log10(magnitudeNorm);

phaseShift = atan(wc./w) .* 180./pi;

figure
subplot(2,1,1)
semilogx(w,magnitudeDB)
```

```
ylim([-40,2])
title("Frequency Response Plot of a High-Pass Filter | Brandon Lim U1244501 ")
xlabel("Frequency [Hz]")
ylabel("Magnitude [dB]")
hold on
subplot(2,1,1)
xline(wc)
text(10^3,-30,0,"Fc")

subplot(2,1,2)
semilogx(w,phaseShift)
ylim([-5,100])
xlabel("Frequency [Hz]")
ylabel("Phase Shift [deg]")
hold on
subplot(2,1,2)
xline(wc)
text(10^3,10,"Fc")
```